

# Discussion of the Intermediate test

Saulius Gražulis

Vilnius, 2020


Vilnius University, Faculty of Mathematics and Informatics  
Institute of Informatics



This set of slides may be copied and used as specified in the  
[Attribution-ShareAlike 4.0 International](#) license



# XOR gate

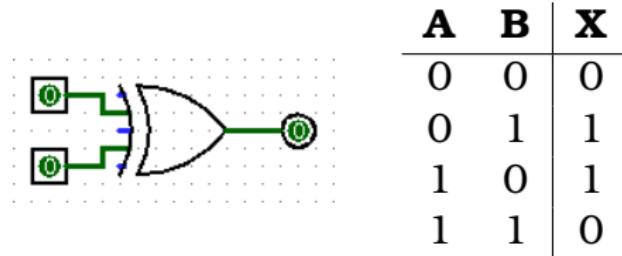


Three interpretations:

- ① One and only one input active
- ② Odd number of inputs active
- ③ Inputs are not equivalent

All three interpretations are the same for 2 inputs...

# Multi-input XOR gate

... but not for 3 and more inputs ...

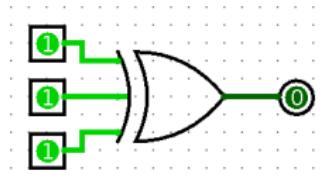

A	B	C	X	
One of three XOR <sup>1</sup>			Odd no. of inputs $A \oplus B \oplus C^2$	Non-equivalence $A \not\equiv B \vee B \not\equiv C$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	<b>0</b>	<b>1</b>

<sup>1</sup>Logisim

<sup>2</sup>Circuit manufacturers

# IC manufacturer's interpretation

$$A \oplus B \oplus C$$

Nexperia

**74LVC1G386**

3-input EXCLUSIVE-OR gate

## 5 Functional diagram

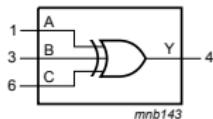


Figure 1. Logic symbol

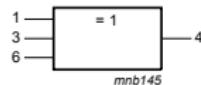


Figure 2. IEC logic symbol

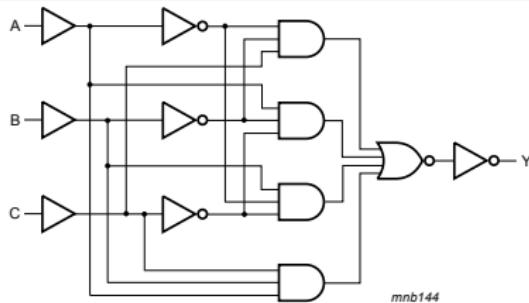


Figure 3. Logic diagram

# IC manufacturer's interpretation

$$A \oplus B \oplus C$$

Nexperia

**74LVC1G386**


3-input EXCLUSIVE-OR gate

Table 4. Function table [1]

Input			Output
A	B	C	Y
L	L	L	L
L	L	H	H
L	H	L	H
L	H	H	L
H	L	L	H
H	L	H	L
H	H	L	L
H	H	H	H

[1] H = HIGH voltage level;  
L = LOW voltage level

# Logisim interpretation

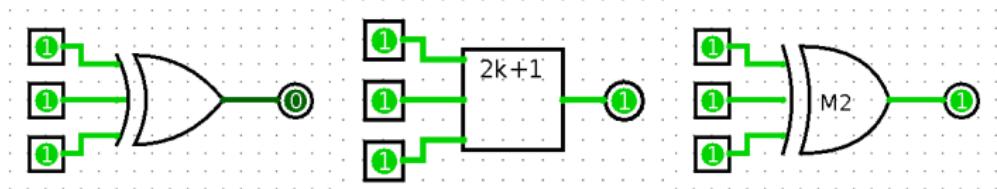


*But if there are more than two specified inputs, the XOR gate will emit 1 only when there is exactly one 1 input, whereas the Odd Parity gate will emit 1 if there are an odd number of 1 inputs.*

<http://www.cburch.com/logisim/docs/2.1.0/libs/gates/xor.html>

# Gray codes

<b>Number</b>	<b>Gray code</b>	<b>Binary positional</b>
0	0000	0000
1	0001	0001
2	0011	0010
3	0010	0011
4	0110	0100
5	0111	0101
6	0101	0110
7	0100	0111
8	1100	1000
9	1101	1001
A	1111	1010
B	1110	1011
C	1010	1100
D	1011	1101
E	1001	1110
F	1000	1111

# Uses of Gray code

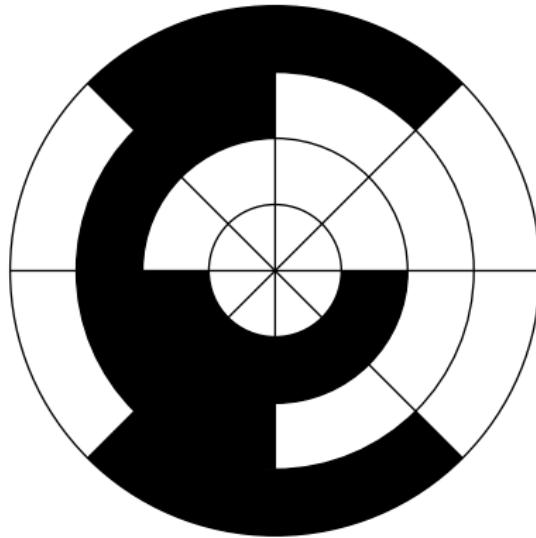

By jjbeard - Encoder\_disc.png, Public Domain

# Deciphering assembler

LDC D1

ST A1

LDC D2

ST A2

LD A1

SUB A2

LDC 12

ST 20

LDC 14

ST 21

LD 20

SUB 21


- $A \leftarrow 12$
- $A \rightarrow [20]$ ; [20] is now 12
- $A \leftarrow 14$
- $A \rightarrow [21]$ ; [21] is now 14
- $A \leftarrow [20]$ ; A is now 12
- $A \leftarrow A - [21]$ ; A is now  $12 - 14$

**Answer:**

$$12 - 14 = -2 = \text{FFFE}_{16}$$

# Active signals during instruction execution

Instruction: LDC → opcode: **02000B**

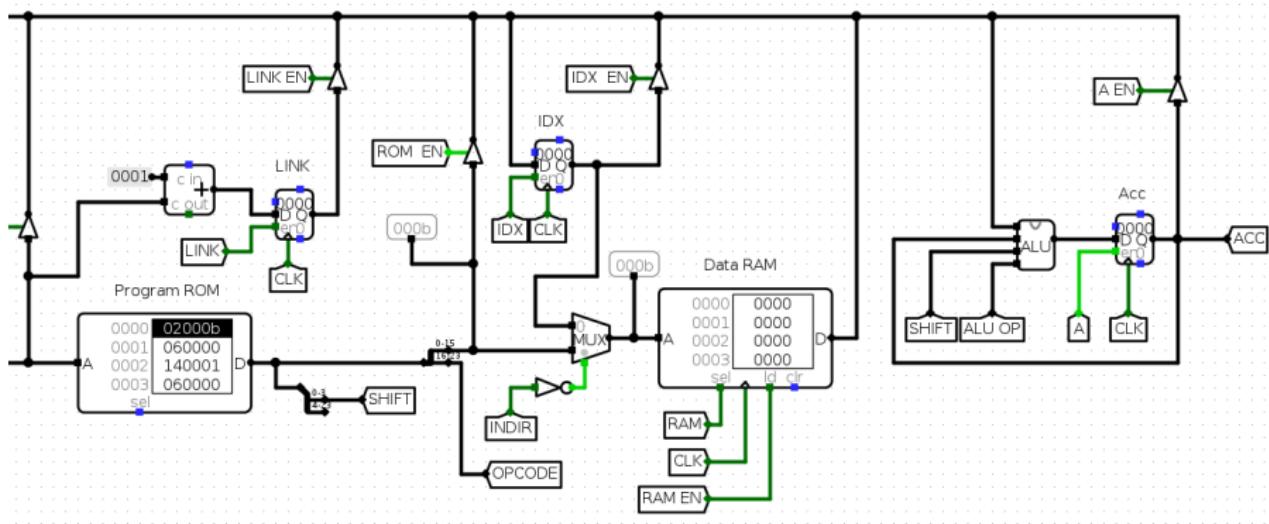

# Conversion of number systems

- quaternary (base-4) → hexadecimal

$$4^2 = 16$$

$$01\ 21\ 33\ 10\ 22_4 \rightarrow 19F4A_{16}$$

- binary → quaternary (base-4)
- ternary → nonary (base-9)